

## Experiment No.:06

**Name of the Experiment:** Half-Wave and Full-Wave Controller Rectifier Circuit with PI controller and P&O Method with Fixed and Variable Step Size

**Objectives:**

- To Use PI Controller to Generate Gate Pulse for Half-Wave and Full-Wave Controlled Rectifier Circuit
- To Learn and Implement of MATLAB Function Code Synchronization Per Cycle of Waveform
- To develop a Controller of Fixed Pulse Algorithm and Variable Pulse Algorithm and Implement on Half-Wave and Full-Wave Circuit

**Software Package:**

- MATLAB
- Simulink

**Half-Wave Controlled Rectifier (PI Controller):**

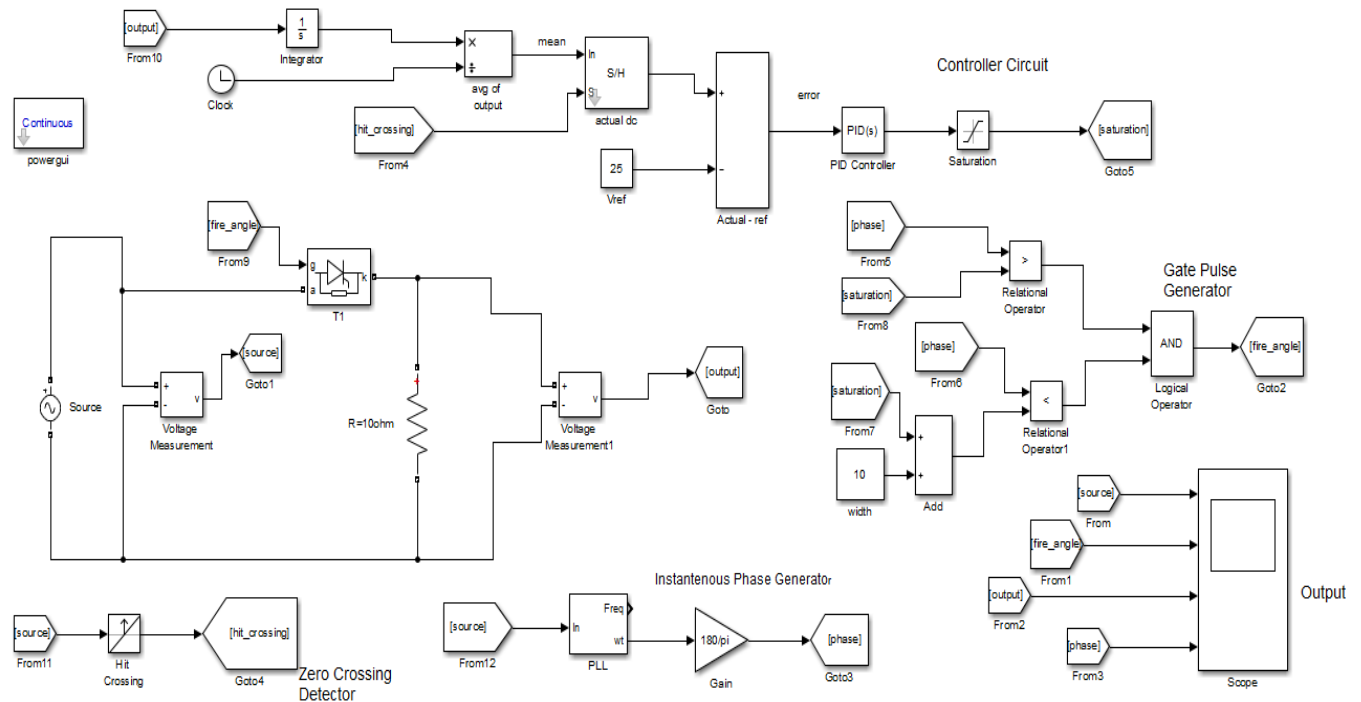


Figure 1.1.: Half Wave Controlled Rectifier Circuit with PI Controller to Achieve Reference Voltage = 25V in Simulink

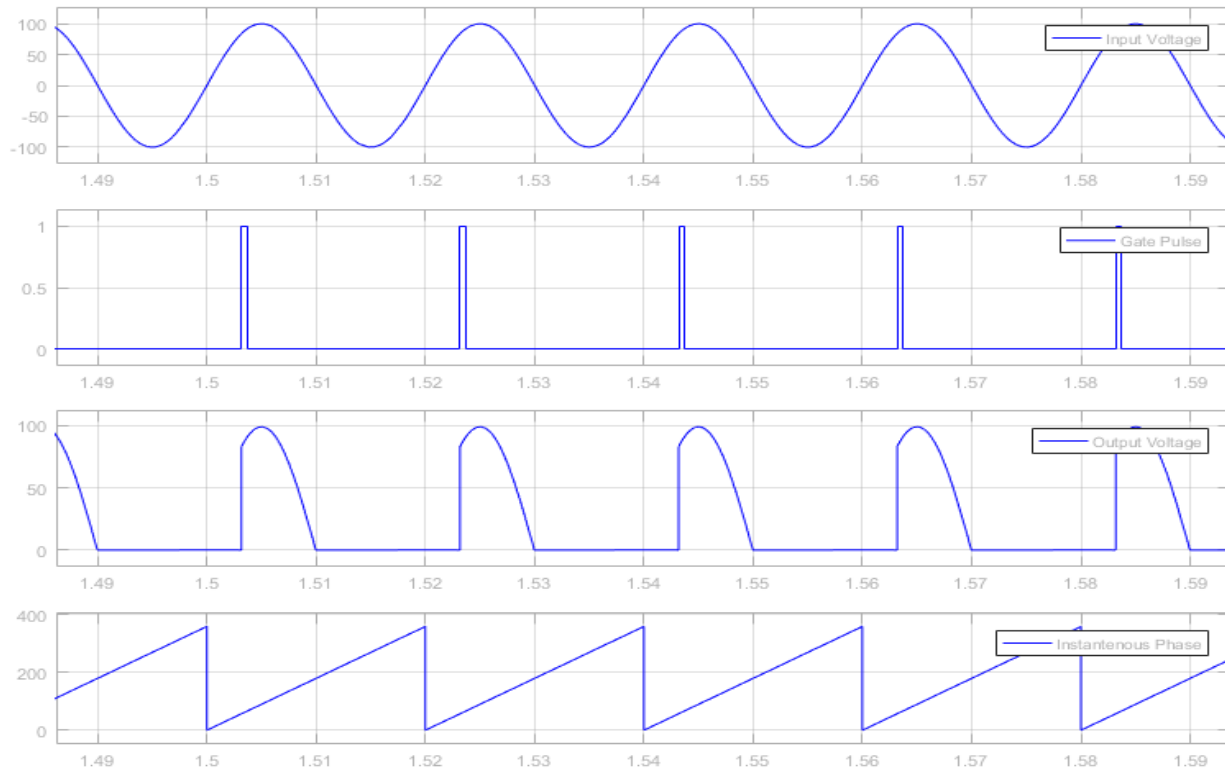


Figure 1.2.: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Half -Wave Controlled Rectifier Circuit with PI Controller ( $V_{ref} = 25V$ ) in Simulink

### Half-Wave Controlled Rectifier with Fixed Step Size (P & O method):

MATLAB CODE for Fixed Step-Size:

```

TriggedSubsystem/MATLAB Function  X  +
1  function updated_alpha = Fixed_Controller(difference)
2  -   step_size = 5;
3  -   persistent alpha;
4  -   if isempty(alpha)
5  -       alpha = 0;
6  -   end
7  -   if difference > 0
8  -       updated_alpha = alpha + step_size;
9  -       alpha = updated_alpha;
10 -   elseif difference < 0
11 -       updated_alpha = alpha - step_size;
12 -       alpha = updated_alpha;
13 -   else
14 -       updated_alpha = alpha;
15 -   end
16 - end

```

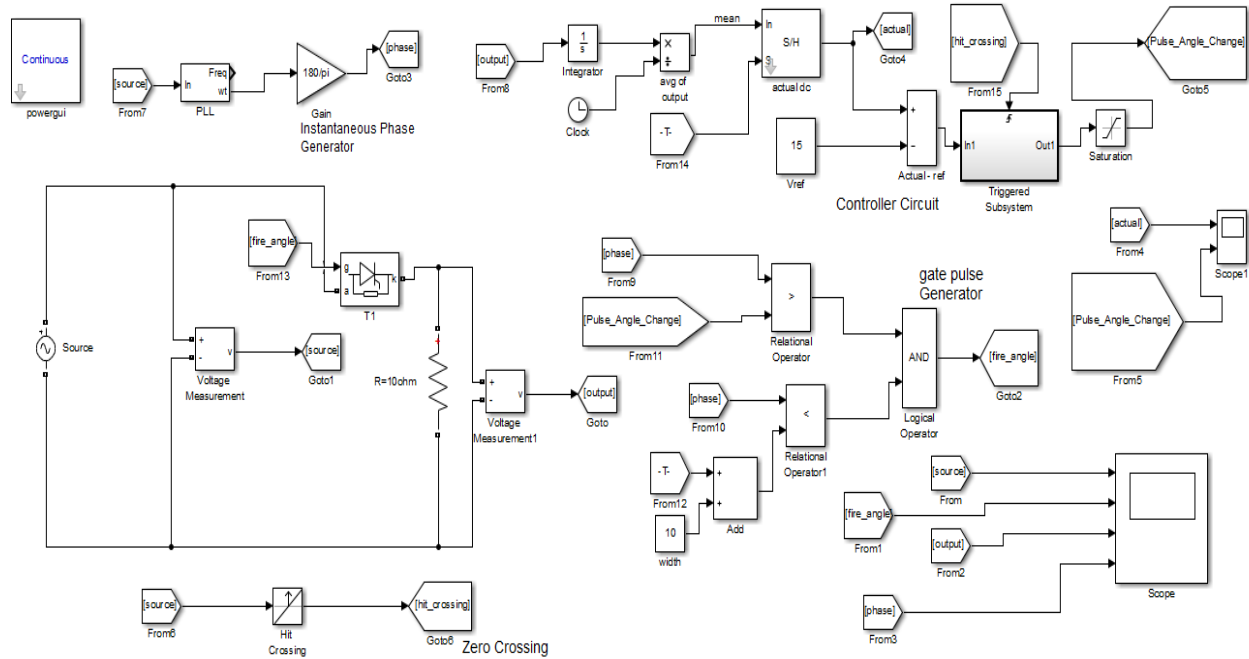


Figure1.3.: Half-Wave Controlled Rectifier with Fixed Step Size (P & O method) where  $V_{ref} = 15V$  in Simulink

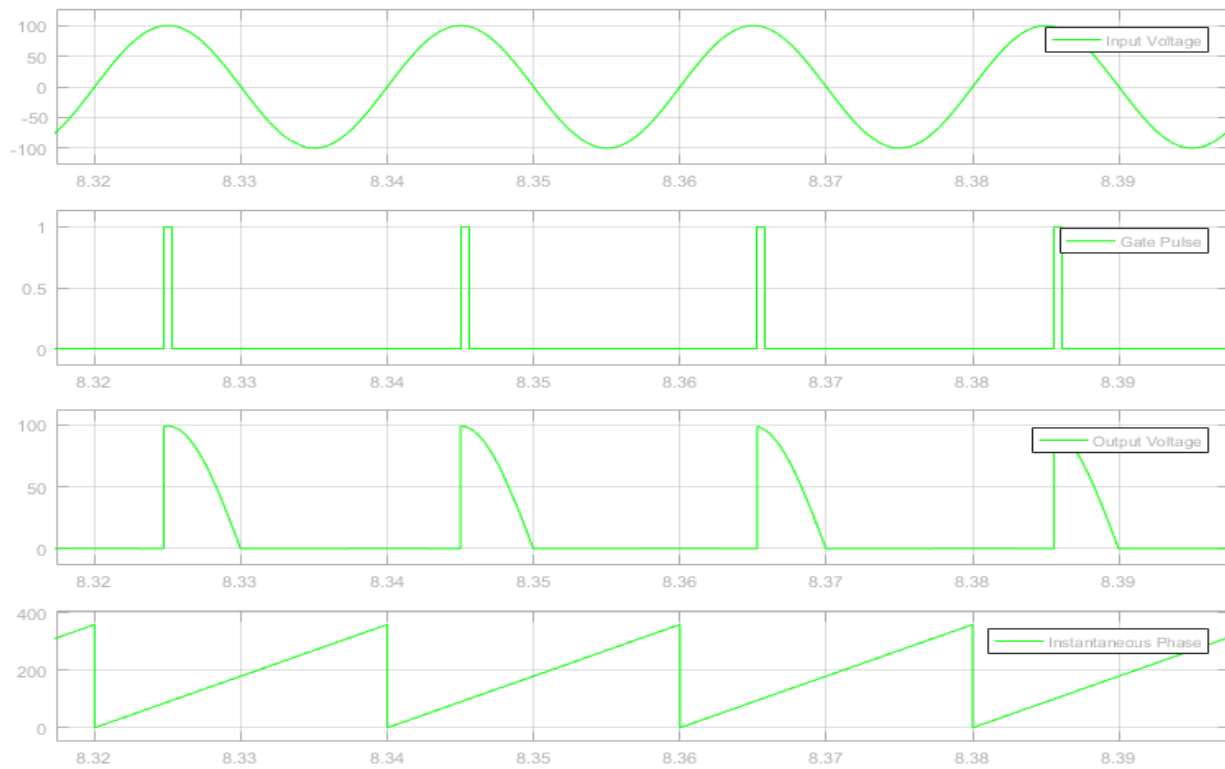


Figure1.4.: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Half -Wave Controlled Rectifier Circuit with Fixed Step Size (P & O method) with  $V_{ref} = 15V$  in Simulink

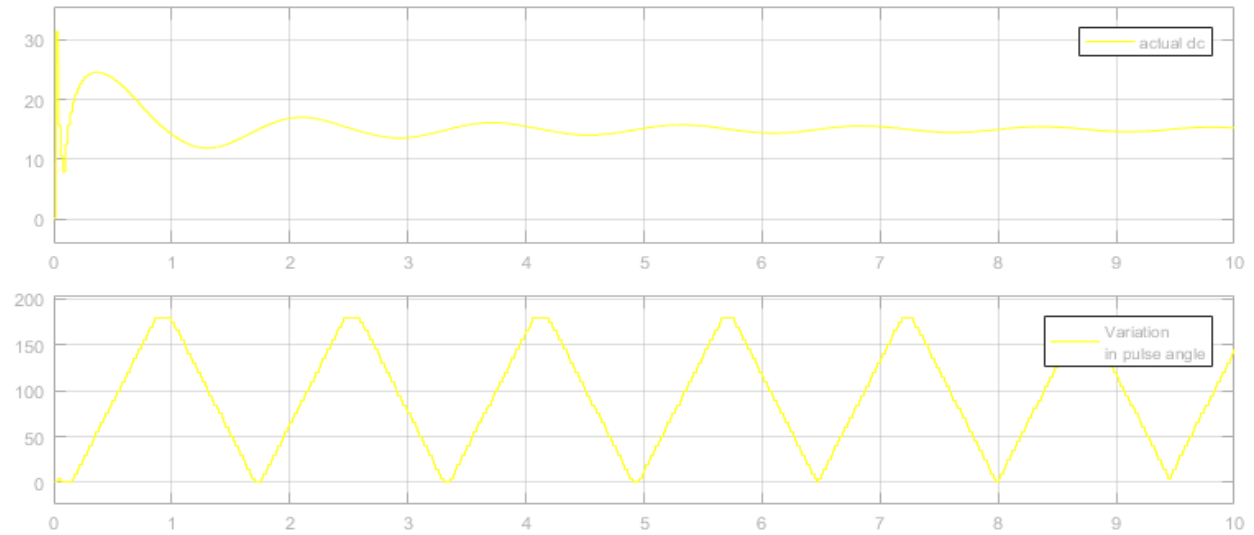


Figure 1.5.: Actual dc and Variation in Pulse angle waveform in of Half -Wave Controlled Rectifier Circuit with Fixed Step Size (P & O method) in Simulink

### Half -Wave Controlled Rectifier Circuit with Variable Step Size (P & O method):

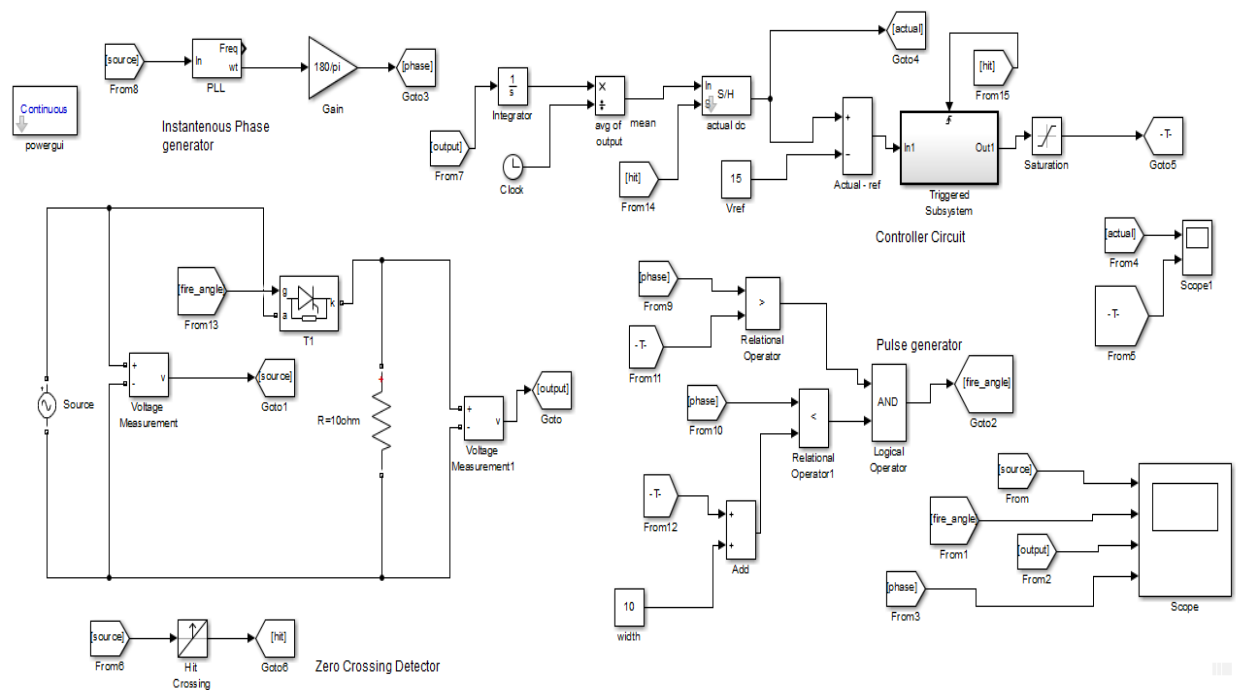


Figure1.6.: Half-Wave Controlled Rectifier with Variable Step Size (P & O method) where Vref = 15V in Simulink

### MATLAB CODE for Variable Step Size:

```
1 function updated_alpha = Variable_Controller(difference)
2     if difference > 10
3         step_size = 15;
4     elseif difference < 10 && difference > 5
5         step_size = 10;
6     else
7         step_size = 5;
8     end
9     persistent alpha;
10    if isempty(alpha)
11        alpha = 0;
12    end
13    if difference > 0
14        updated_alpha = alpha + step_size;
15        alpha = updated_alpha;
16    elseif difference < 0
17        updated_alpha = alpha - step_size;
18        alpha = updated_alpha;
19    else
20        updated_alpha = alpha;
21    end
22 end
```

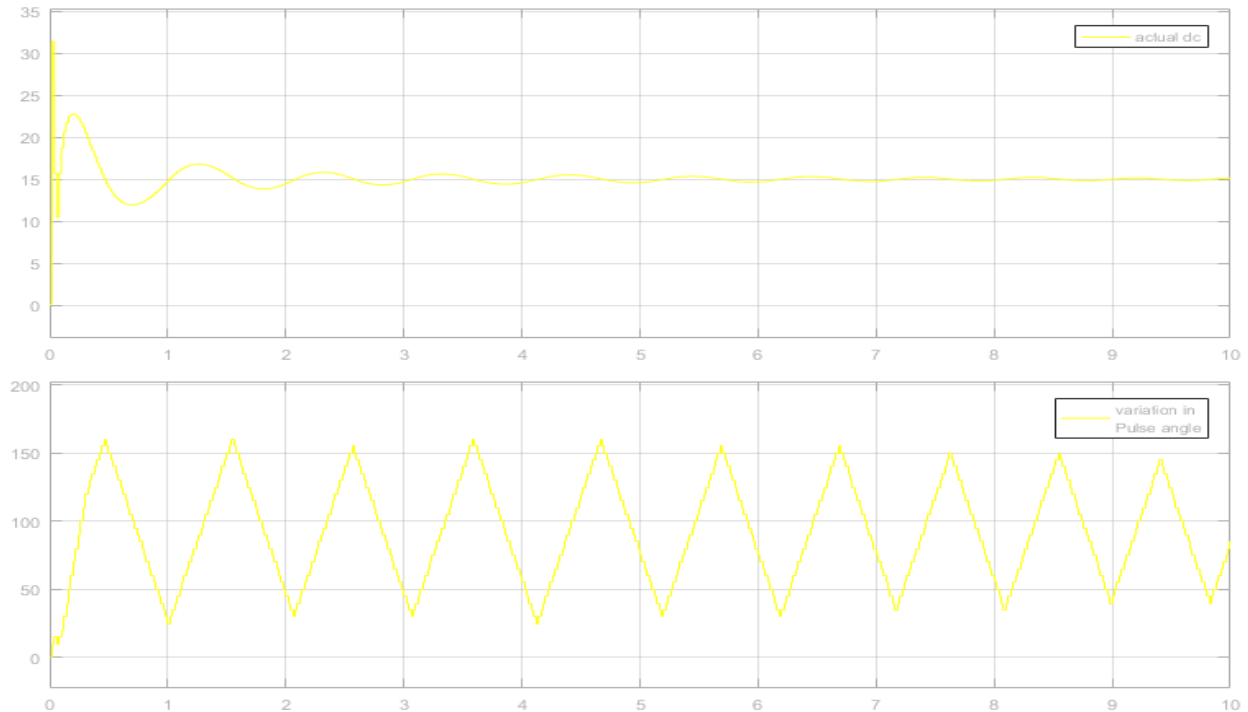


Figure 1.7.: Actual dc and Variation in Pulse angle waveform in of Half -Wave Controlled Rectifier Circuit with Variable Step Size (P & O method) in Simulink

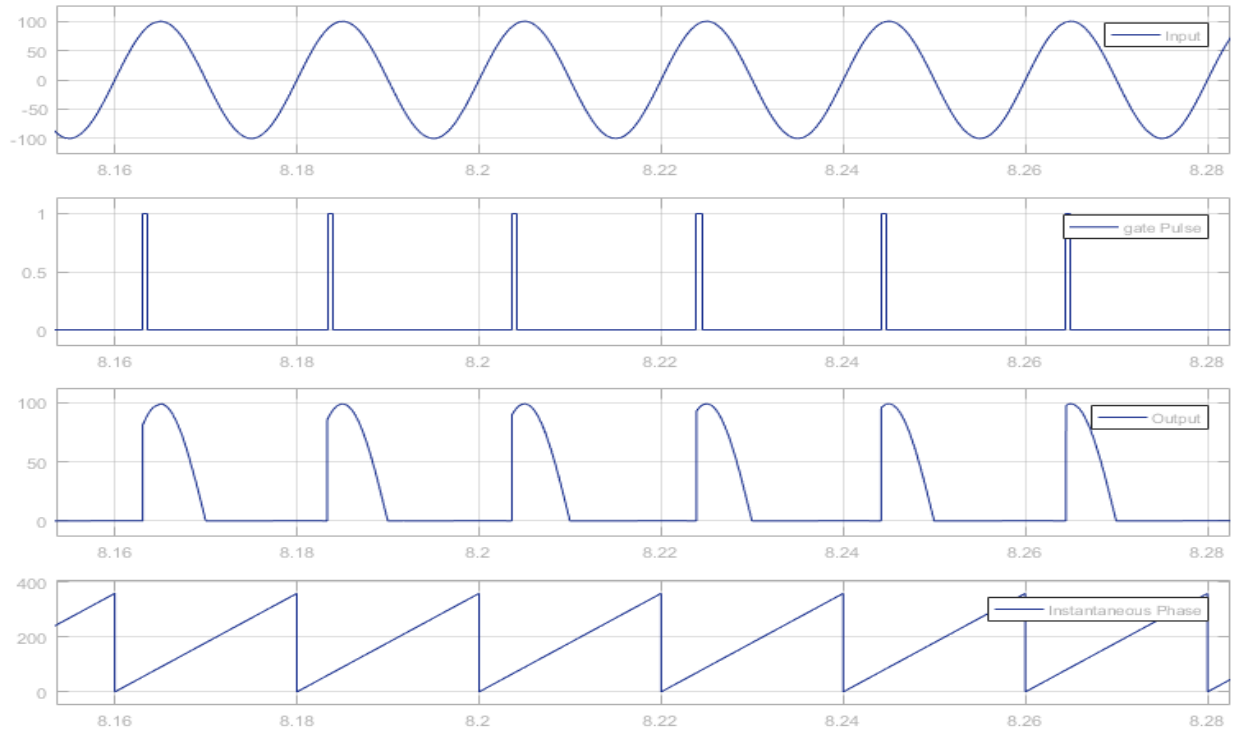


Figure 1.8.: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Half -Wave Controlled Rectifier Circuit with Variable Step Size (P&O method) with  $V_{ref} = 15V$  in Simulink

### Full-Wave Controlled Rectifier with PI Controller:

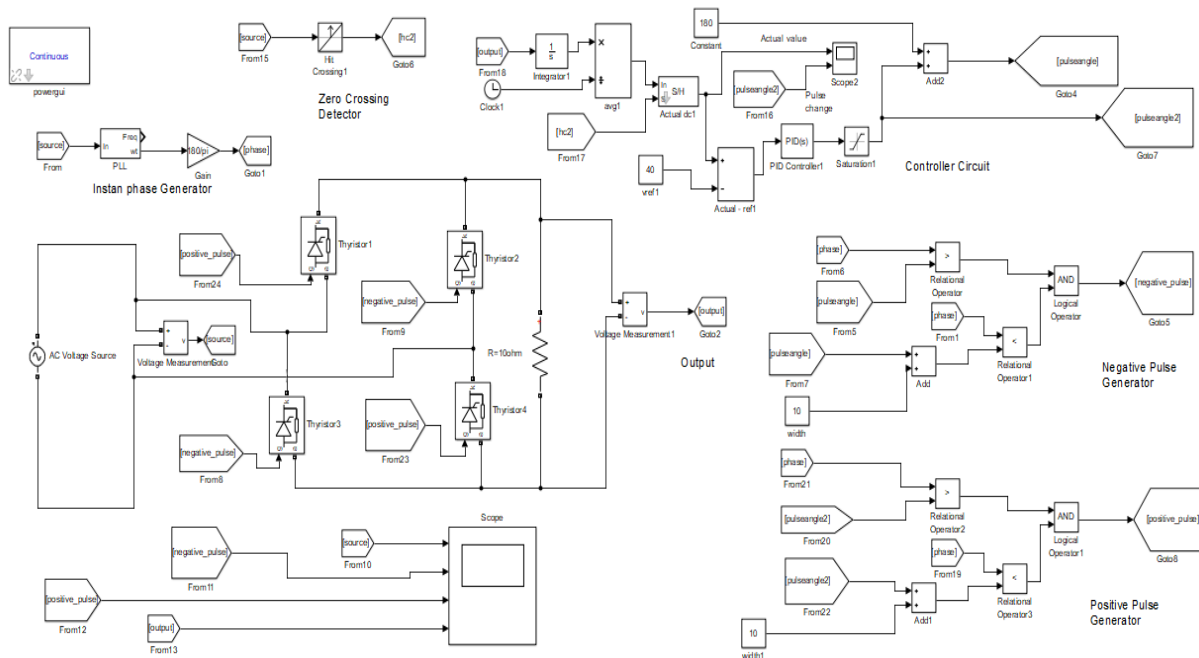


Figure 1.9.: Full Wave Controlled Rectifier Circuit with PI Controller to Achieve Reference Voltage = 40V in Simulink

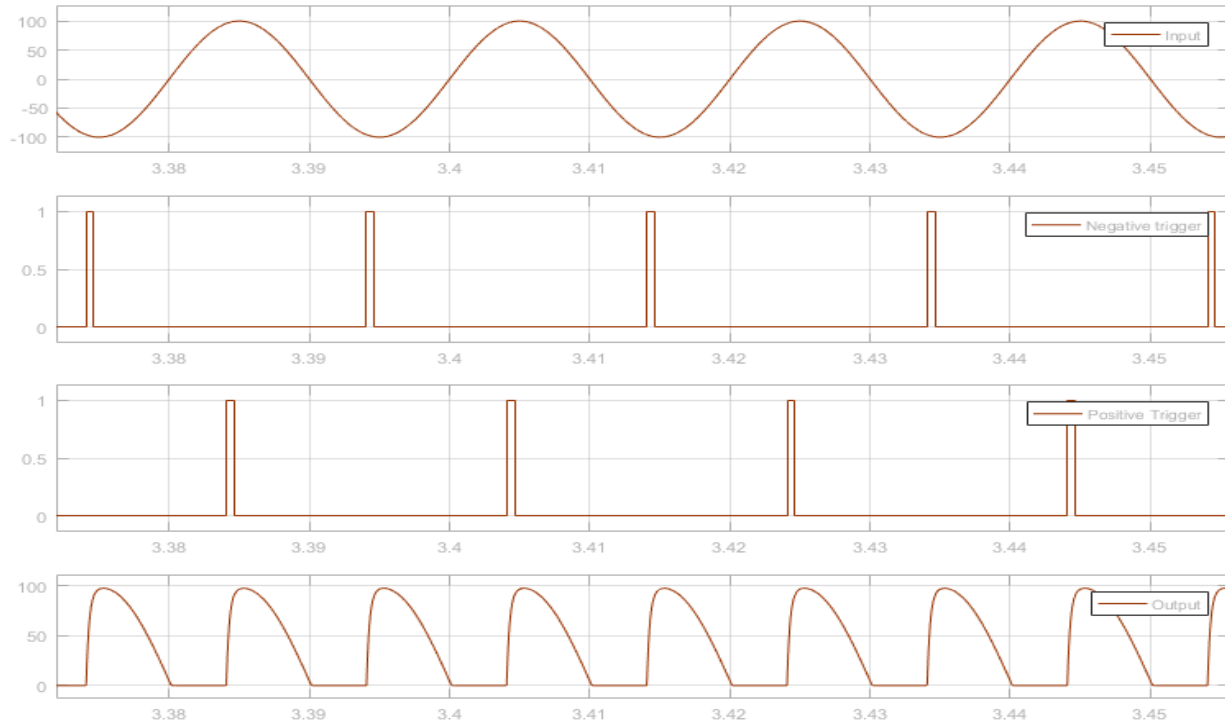


Figure 1.10: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Full -Wave Controlled Rectifier Circuit with PI Controller ( $V_{ref} = 40V$ ) in Simulink

### Full-Wave Controlled Rectifier with fixed Step Size (P&O Method):

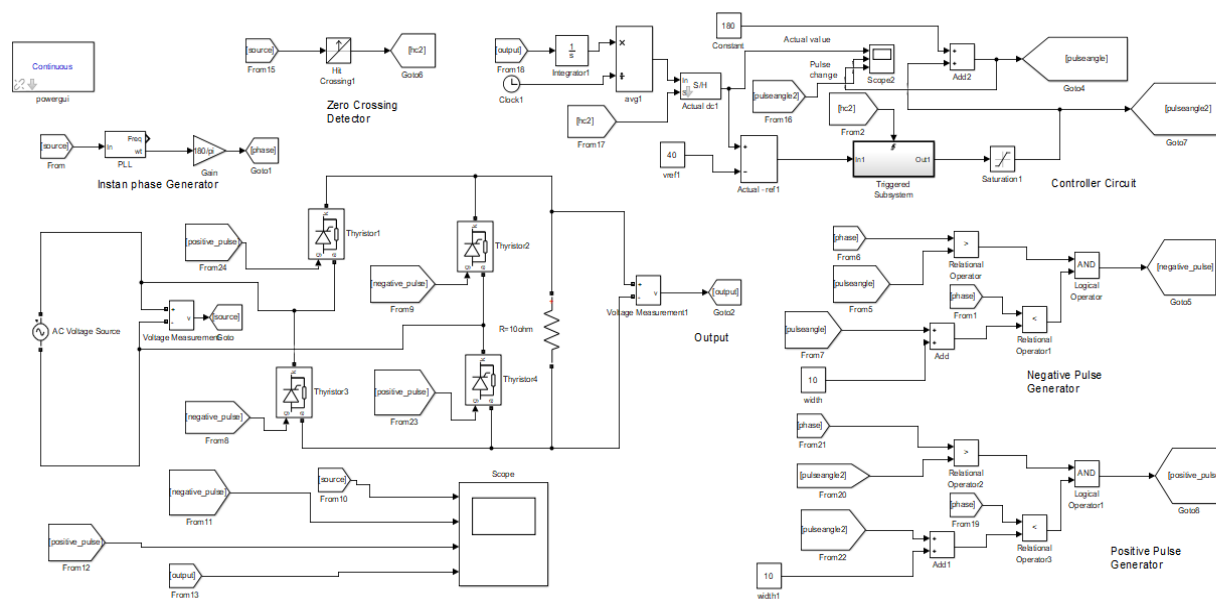


Figure1.11.: Full-Wave Controlled Rectifier with Fixed Step Size (P & O method) where  $V_{ref} = 40V$  in Simulink

MATLAB CODE for fixed Step Size:

```

TriggeredSubsystem/MATLAB Function  X  +
1  function updated_alpha = Fixed_Controller(difference)
2  -  step_size = 5;
3  -  persistent alpha;
4  -  if isempty(alpha)
5  -      alpha = 0;
6  -  end
7  -  if difference > 0
8  -      updated_alpha = alpha + step_size;
9  -      alpha = updated_alpha;
10 -  elseif difference < 0
11 -      updated_alpha = alpha - step_size;
12 -      alpha = updated_alpha;
13 -  else
14 -      updated_alpha = alpha;
15 -  end
16 -  end

```

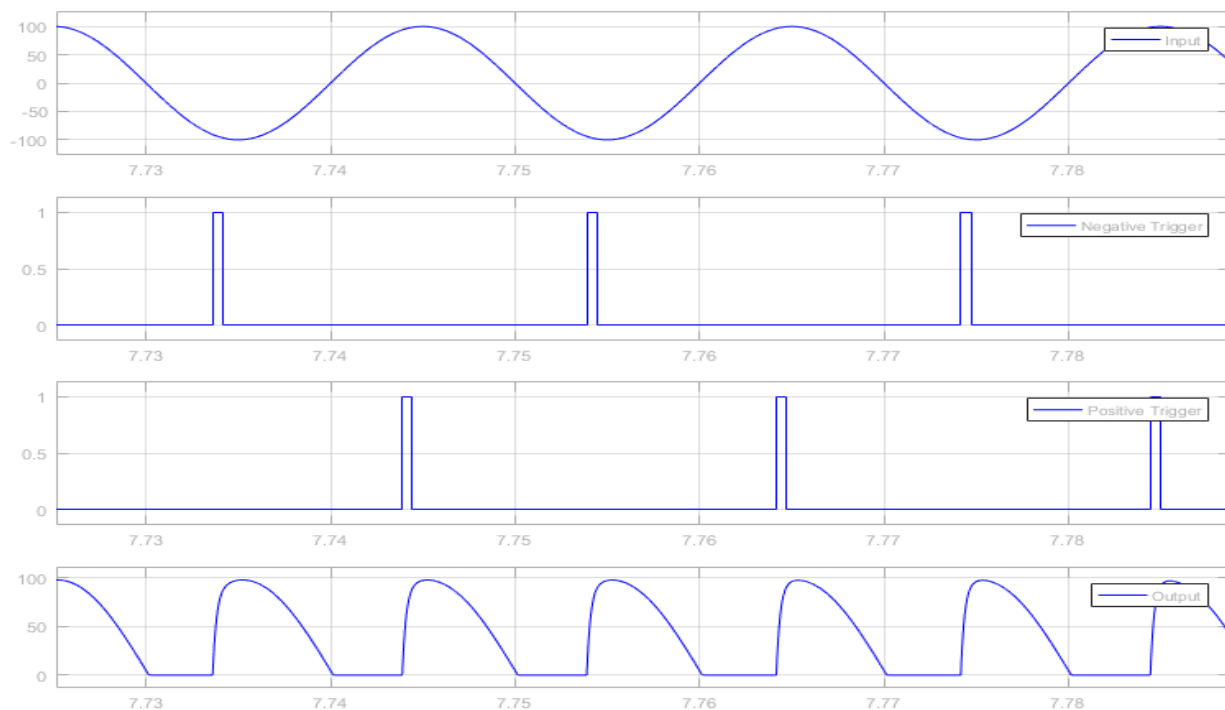


Figure 1.12.: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Full -Wave Controlled Rectifier Circuit with Fixed Step Size (P & O method) with  $V_{ref} = 40V$  in Simulink



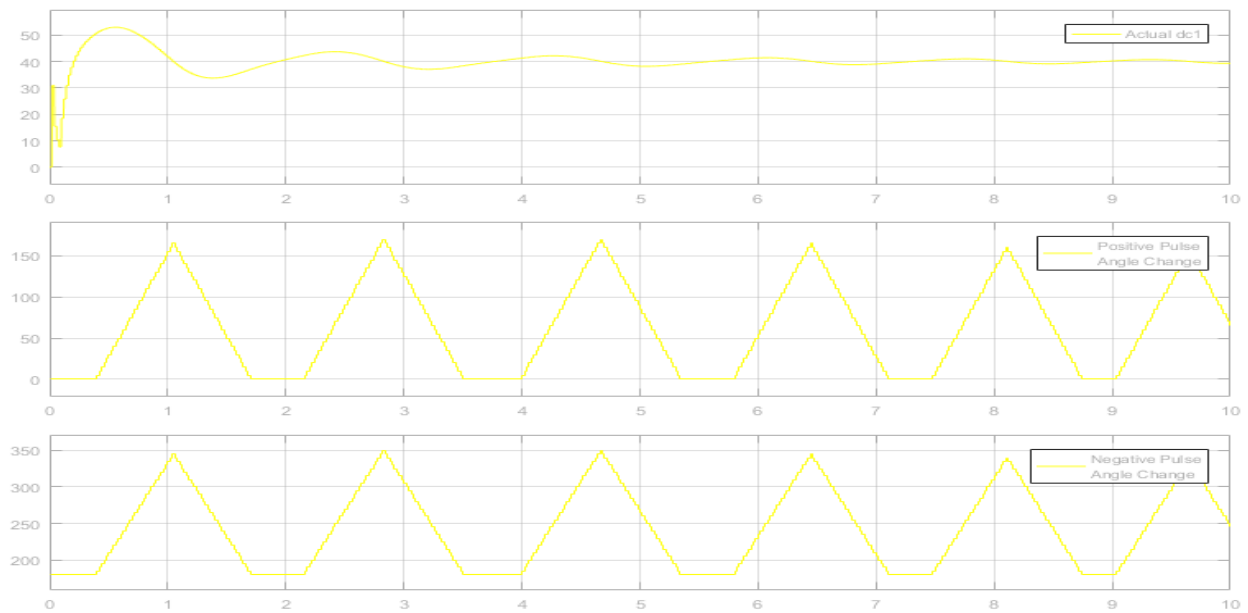


Figure 1.13: Actual dc and Variation in Pulse angle waveform in of Full -Wave Controlled Rectifier Circuit with Fixed Step Size (P & O method) in Simulink

### Full-Wave Controlled Rectifier with Variable Step Size (P&O Method):

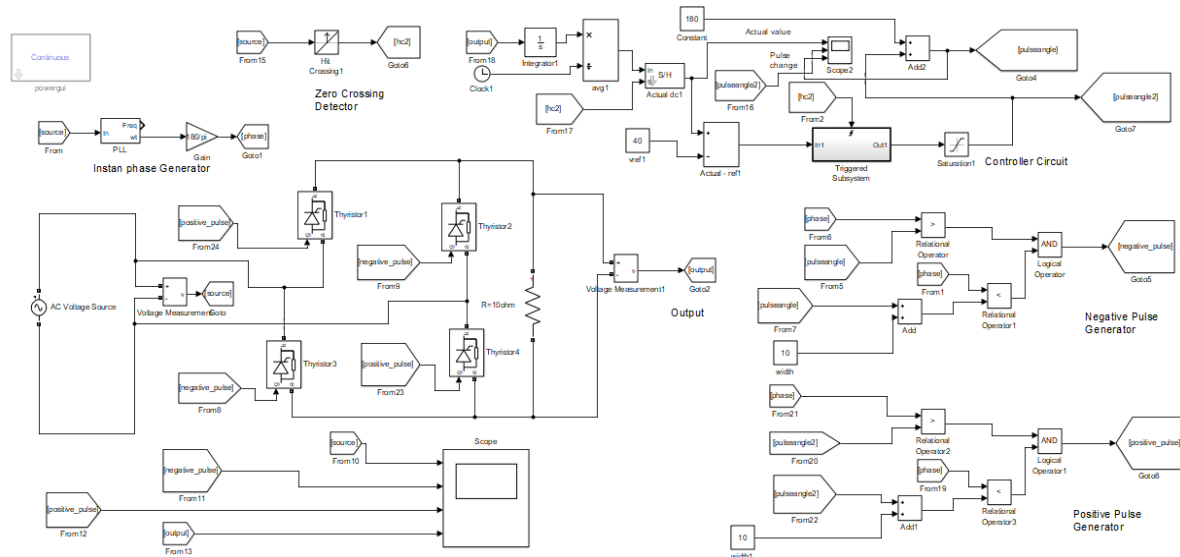


Figure 1.14.: Full-Wave Controlled Rectifier with Variable Step Size (P & O method) where  $V_{ref} = 40V$  in Simulink

MATLAB CODE for Variable Step Size:

```

1  function updated_alpha = Variable_Controller(difference)
2  -   if difference > 10
3  -       step_size = 15;
4  -   elseif difference < 10 && difference > 5
5  -       step_size = 10;
6  -   else
7  -       step_size = 5;
8  -   end
9  -   persistent alpha;
10 -   if isempty(alpha)
11 -       alpha = 0;
12 -   end
13 -   if difference > 0
14 -       updated_alpha = alpha + step_size;
15 -       alpha = updated_alpha;
16 -   elseif difference < 0
17 -       updated_alpha = alpha - step_size;
18 -       alpha = updated_alpha;
19 -   else
20 -       updated_alpha = alpha;
21 -   end
22 - end

```

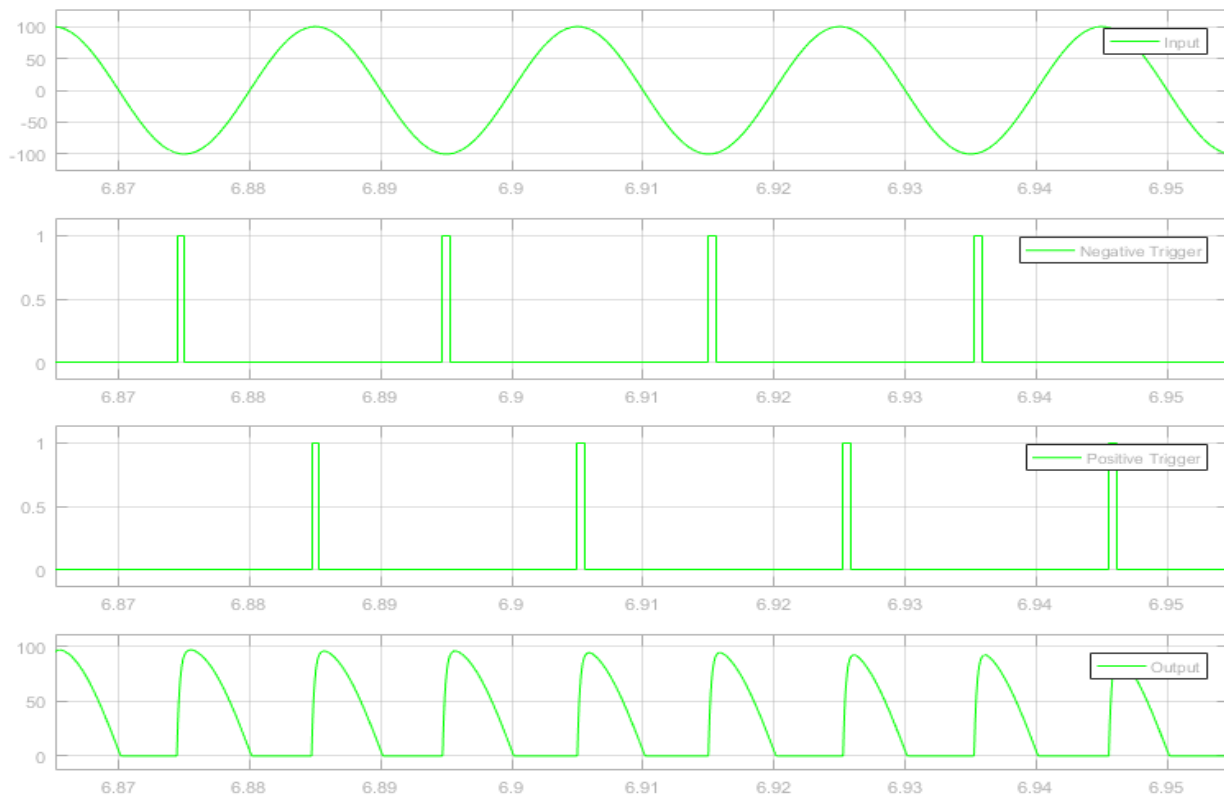


Figure 1.15.: Input, Gate Pulse, Output Voltage and Instantaneous Phase of Full -Wave Controlled Rectifier Circuit with Variable Step Size (P&O method) with  $V_{ref} = 40V$  in Simulink

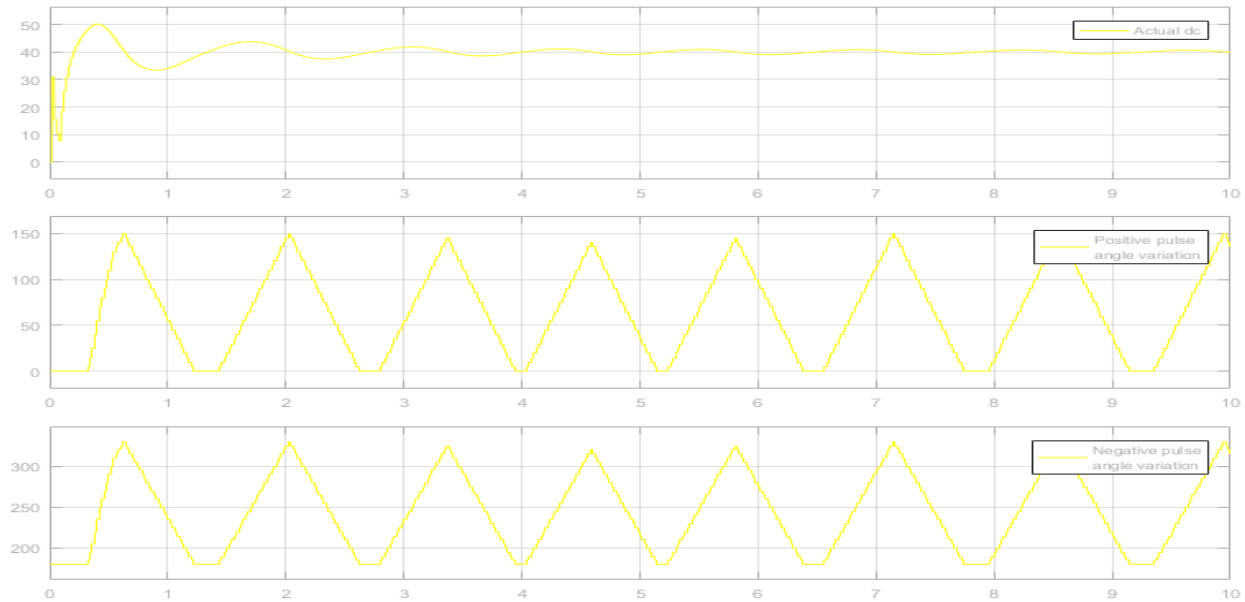


Figure 1.16.: Actual dc and Variation in Pulse angle waveform in of Full -Wave Controlled Rectifier Circuit with Variable Step Size (P & O method) in Simulink

**Result & Discussion:** In this experiment, half-wave and full-wave controlled rectifier circuit was made using PI controller and (P&O) method with fixed and variable step size. By setting the value of  $V_{ref}$  the desired actual dc value was found in the output waveform. These 6 circuits are designed in such a way so that it can give upto maximum convertible dc value in the output where PI controller will automatically fix the firing angle. It can be seen that for different  $V_{ref}$  value different firing angle was set accordingly. Also, it can be seen that for fixed step size the steady state error was more than found in the variable step size which can be compared by observing figure 1.16, 1.13, 1.7, 1.5. For variable step size the steady state error was minimum. In full-wave rectifier circuit the negative pulse was created by phase shifting the positive pulse angle by 180 degree. The experiment was done carefully and the MATLAB codes logics were produced according to the desired circuit. By observing the result or input-output waveform with phase and pulse angle it can be said that the desired value was yielded in this simulation. So, the simulation was done successfully and expected result was found.